

EE619: Project-II

Anubhav Bhatla, 200070008

April 21, 2024

Design for Cross-coupled Oscillator

In order to limit the power below 3mW, we can take I to be **2mA**. Say we choose $L_1 = L_2 = 1\text{nH}$ (if we use a centre-tapped inductor: $L = 2\text{nH}$). The oscillation frequency is given as follows:

$$2\pi \times f_{osc} = \frac{1}{\sqrt{L_1(C_1 + C_{var})}}$$

For an oscillation frequency of 6GHz, we get $C_1 + C_{var} = 700\text{fF}$. Say we choose $C_{var} = 20\text{fF}$ and $C_1 = C_2 = 680\text{fF}$.

We can choose a width $W = 3200\text{nm}$ for M_0 and M_1 in order to get nearly complete current switching with V_{swing} .

In order to scale I_{BIAS} to I requires a width ratio of $I/I_{BIAS} = 10$. Therefore we can use $W = 10\mu\text{m}$ and $1\mu\text{m}$ for M_2 and M_3 respectively.

Table 1 summarizes the final component parameters used. Figure 1 shows the schematic of the VCO along with component parameter annotations and 2 shows the schematic for the testbench used.

MOS Devices	Finger Width	Length	Multipliers	Fingers
M_0	800nm	60nm	1	4
M_1	800m	60nm	1	4
M_2	$5\mu\text{m}$	60nm	1	2
M_3	500nm	60nm	1	2
Passive Components				Value
L				2nH
C_0				20fF
C_1				20fF
C_2				501fF
C_3				501fF
I_{BIAS}				$200\mu A$
V_{DD}				1.2V

Table 1: Component parameters used for the VCO.

1 Schematic

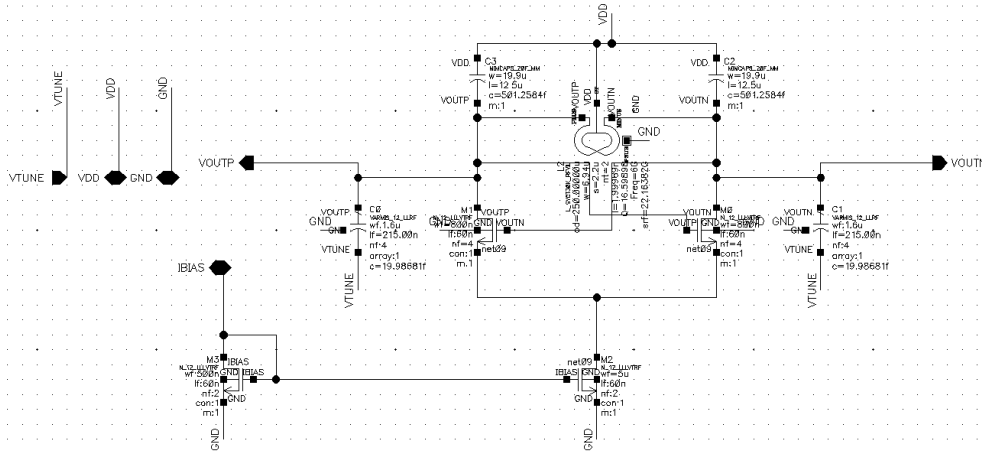


Figure 1: Schematic for the VCO with component parameter annotations.




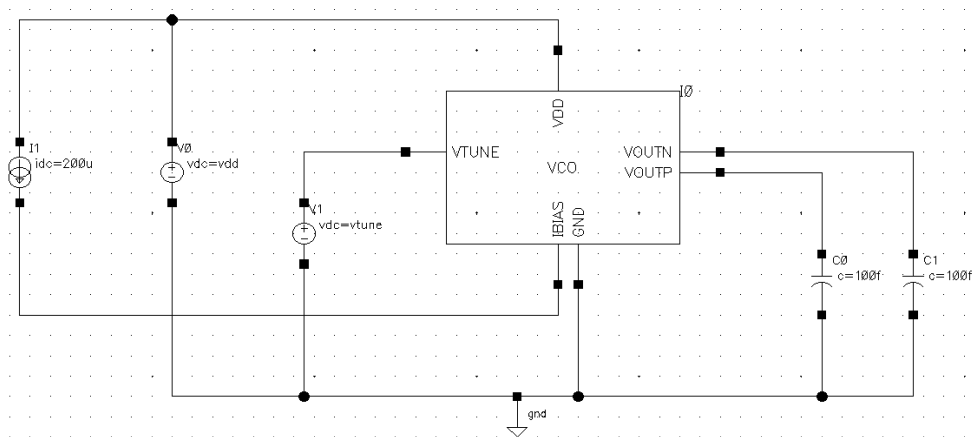
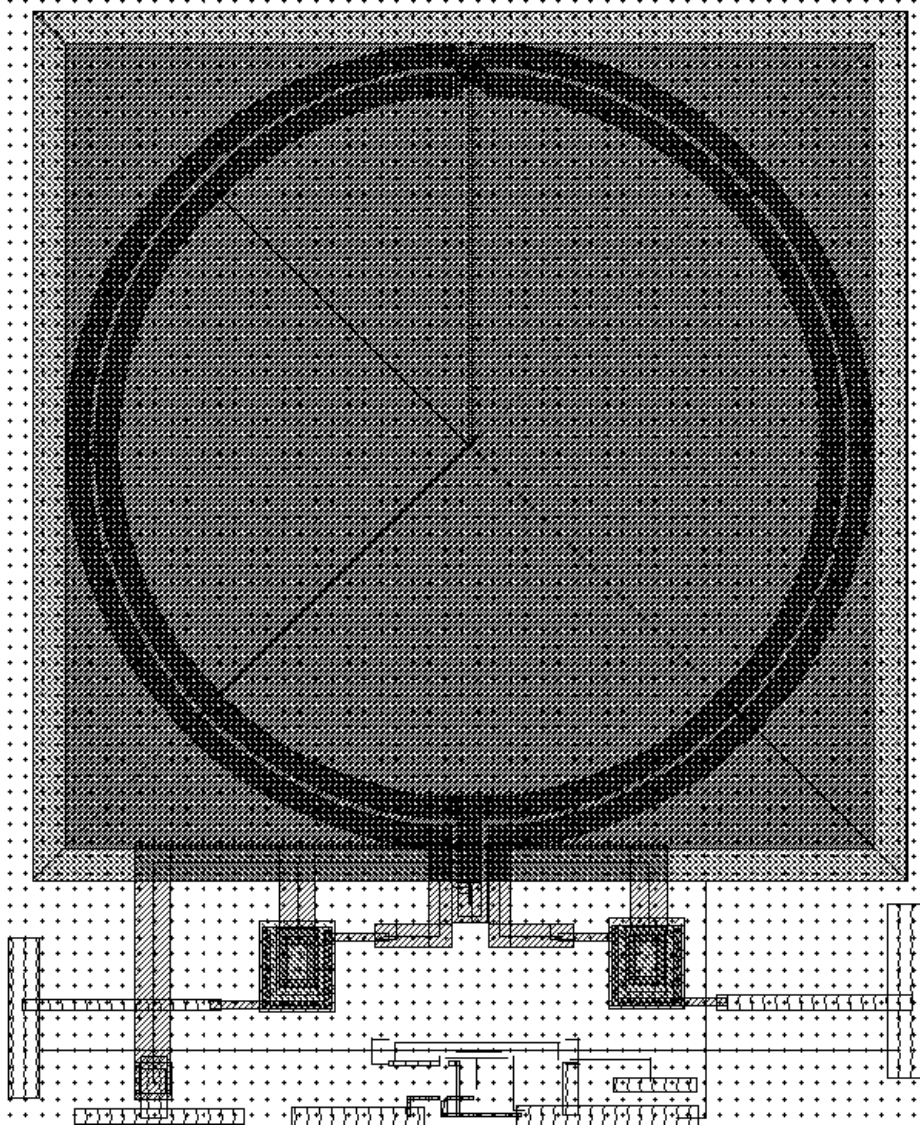


Figure 2: Schematic for the VCO testbench.


2 Layout

 

 


 

3 DRC

 

4 LVS

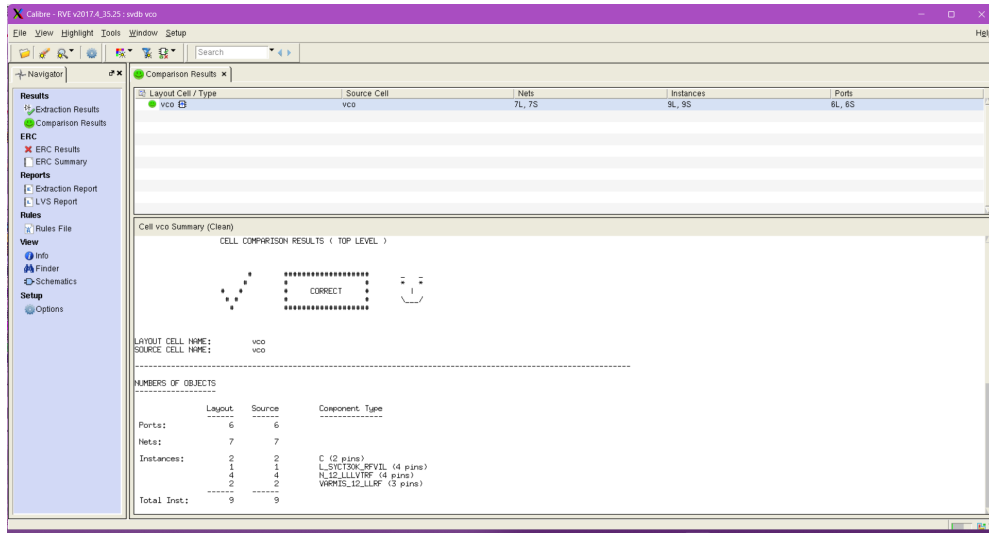

5 Transient

Figure 3 shows the transient signal at the output node of the designed VCO. Here, we can see that we have a peak-to-peak voltage swing of around $1.083V_{pp}$, which meets the required specification.

 


Figure 3: Transient signal at the output node of the VCO.

6 Frequency Tuning

Figure 4 shows the variation of oscillator frequency as V_{tune} varies from 0 to 1.2V. We can observe a tuning range of about **28MHz**. We also observe a max K_{VCO} value of around **61MHz/V**, which is within the required specification. From the schematic simulations, we can observe that the oscillation frequency at $V_{TUNE} = 0.6V$ is around **6.3GHz** and the tuning range is higher, at around **32MHz**. This is because of parasitic capacitances considered in the post-layout simulations, which reduce the oscillation frequency and the tuning range.

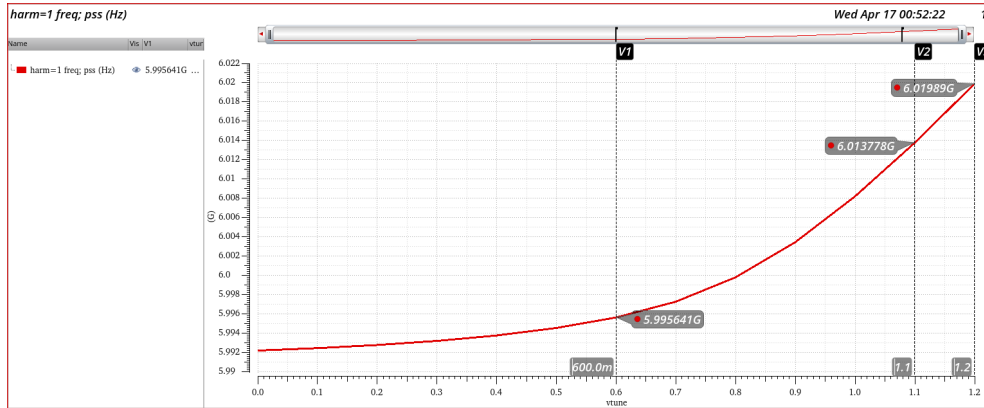


Figure 4: Plot for frequency as V_{tune} varies in post-layout simulations.

 


Figure 5: Plot for frequency as V_{tune} varies in schematic simulations.

7 Phase Noise

Figure 6 shows the phase noise (in dBc) for the designed LNA circuit. The phase noise at a relative frequency of 1MHz is close to -117dBc/Hz , which meets the desired specification.



Figure 6: Phase Noise (in dBc) for the designed VCO circuit.

8 Variation with V_{DD}

Figure 7 shows the variation of oscillator frequency as V_{tune} varies from 1.0 to 1.4V. As we increase V_{DD} , the V_{GS} of the varactors M_2 , M_3 increases. Due to this the capacitance of the varactors also increases as we increase V_{DD} . This leads to a decrease in the oscillation frequency.

 


Figure 7: Plot for frequency as V_{DD} varies.